

26 4. Zero-purity: Sum of products of anyone row or column of S -matrix multiplied by the complex conjugate of the corresponding elements of any other row or column is zero.

$$\sum_{i=1}^n S_{ik} S_{ij}^* = 0 \quad \text{where } k = 0, 1, 2, \dots, n \\ j = 0, 1, 2, \dots, n$$


as all the rows or columns are zero.

∴ For a 2×2 -matrix, if we consider 1st row & 2nd column

$$S_{11} S_{21}^* + S_{12} S_{22}^* = 0$$

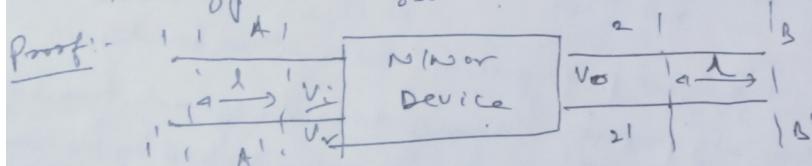5. phase-shifting property :-

Reference plane in passive device shifts due to o.c./s.c., frequency change etc. Under these conditions magnitude of S -parameter remains same but only phase changes.



(1-1'), (2-2') Initial ref planes

(A-A'), (B-B') New ref planes


For initial ref plane $V_r = SV_i$

If planes drift by a distance of ' l ', then voltages experience a phase change of $\pm \beta l$

$$\text{i.e. } V_r e^{j\beta l} = SV_i e^{-j\beta l}$$

$$\text{or } V_r = S' V_i \quad \text{where } S' = S e^{-j\beta l} \quad (1)$$

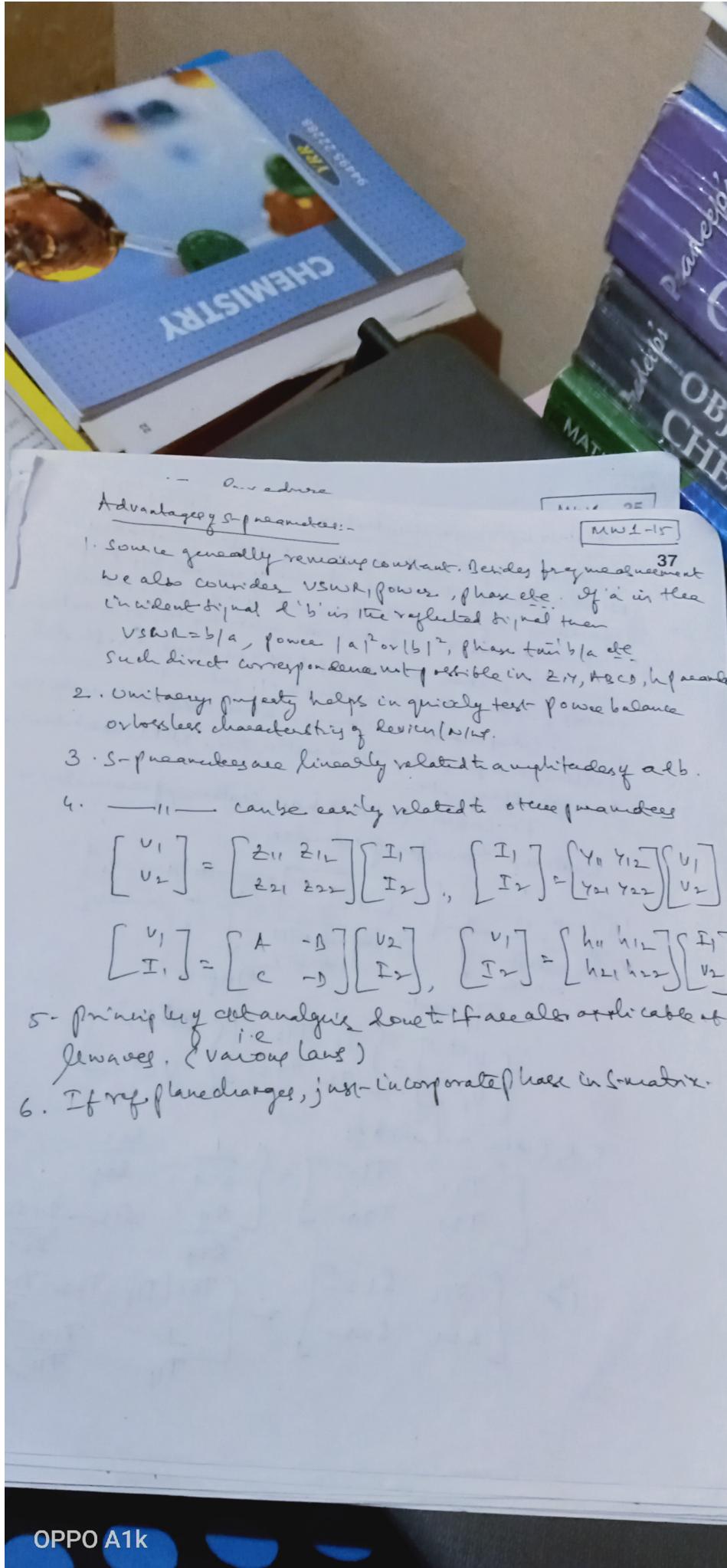From (1) it is clear that Mag of S remains same but phase



-- Procedure

MW1- 35


38 T-Matrix or Transmission Matrix

MW1- 16

This is useful in studying the property cascaded N/W stages. T-matrix directly relates S/P & off parameters. If we multiply matrix of individual N/W in cascade we get overall matrix of the combination.

T-matrix relates S/P port incident & reflected waves (Independent Variables) to off port \rightarrow (Dependent Variables). It is useful in analyzing filters, amplifiers, Transmitters etc., SDR (Super heterodyne receiver) stages etc.

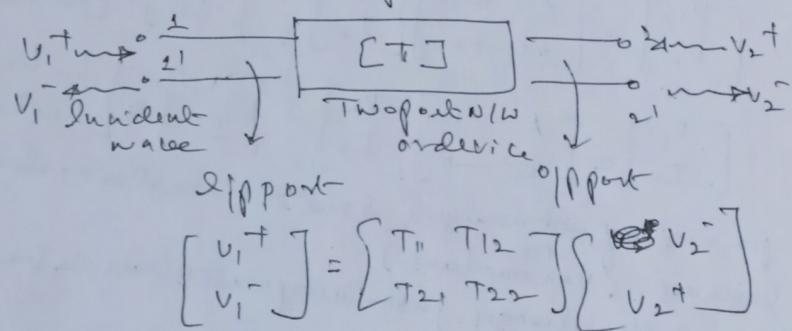T-contributes chain scattering parameter or Scattering transfer parameters.




$$\begin{bmatrix} V_1^+ \\ V_1^- \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} V_2^+ \\ V_2^- \end{bmatrix}$$

S & T are related as,

$$\begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{S_{21}} & \frac{S_{22}}{S_{21}} \\ \frac{S_{11}}{S_{21}} & S_{12} - \frac{S_{11}S_{22}}{S_{21}} \end{bmatrix}$$
$$\text{or } \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} T_{21}/(T_{11}T_{22}-T_{21}T_{12}) & \frac{T_{12}}{T_{11}} \\ \frac{1}{T_{11}} & \frac{T_{12}}{T_{11}} \end{bmatrix}$$

MW1 - 35

MW1 - 17

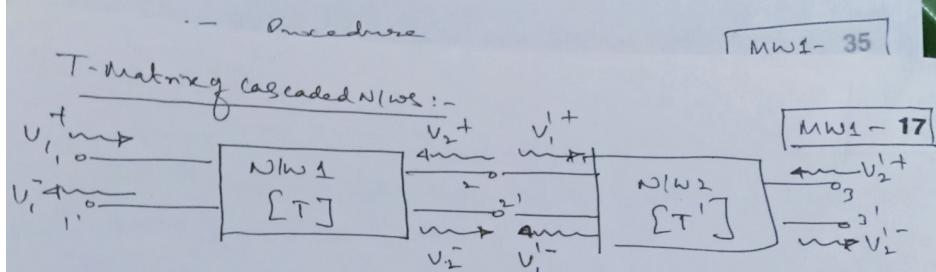

$$\text{At junction } 2-2': \quad v_2^+ = v_1^- \quad \text{and} \quad v_2^- = v_1^+ \quad (1)$$

$$\text{W.L.C.T for } N/W_2 \quad \begin{bmatrix} v_1^+ \\ v_1^- \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} v_2^+ \\ v_2^- \end{bmatrix} \quad (2)$$

$$\text{W.L.C.T for } N/W_1 \quad \begin{bmatrix} v_1^+ \\ v_1^- \end{bmatrix} = \begin{bmatrix} T_{11}' & T_{12}' \\ T_{21}' & T_{22}' \end{bmatrix} \begin{bmatrix} v_2^+ \\ v_2^- \end{bmatrix} \quad (3)$$

Eq (3) in eq (2) gives

$$\begin{bmatrix} v_1^+ \\ v_1^- \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} T_{11}' & T_{12}' \\ T_{21}' & T_{22}' \end{bmatrix} \begin{bmatrix} v_2^+ \\ v_2^- \end{bmatrix}$$

$$\text{LHS} = \boxed{T}_{\text{TOT}} \begin{bmatrix} v_2^+ \\ v_2^- \end{bmatrix}$$

$$\text{where } \boxed{T}_{\text{TOT}} = \boxed{T} \boxed{T'} \boxed{T'}$$

This can be extended for n stages

Microwave Filters:-


"They are two-port, reciprocal, passive, linear devices which attenuate heavily the unwanted signal frequencies while passing desired frequencies".

There are three types:-

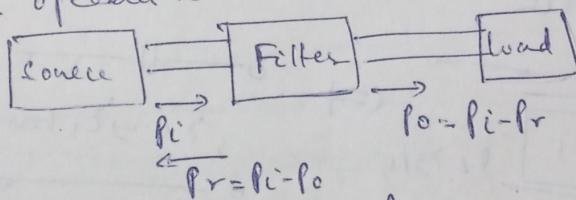- 1) * Reflective type or Insertion loss type:- uses cap & induct elements producing ideally zero reflection & high atten. in S.B.
- 2) * Absorptive type:- They dissipate unwanted signal internally & pass the wanted signal.
- 3) * Lossy filter:- Uses lossy material to produce heavy loss for rejected signal & less loss for wanted signal.

Here we consider only first type.

Microwave filter operates between a source & a load of 50Ω .



$$\text{Insertion loss} = IL_{dB} = 10 \log \frac{Pi}{Po} = 10 \log \frac{Pi}{Pi - Pr} = 10 \log \frac{1}{1 - |F|^2}$$

where F will be Volt refl. coeff. = $\sqrt{Pr/Pi}$

$$\text{Return loss} = 10 \log \frac{Pi}{Pr} = 10 \log \frac{1}{|F|^2}$$

Microwave filter parameters - Design parameters are insertion loss,

Return loss, Group delay, Pass band att., f_c,






OPPO A1k \Rightarrow f_1/f_2 impedances, order of filter, Slope

OCT 2018: Procedure
 Design of wave filters by
 - Chebyshev
 - Butterworth
 - RIAE filters for design
 related to other

Ques 22 Group delay (T_d) is important for multi frequency or pulsed signals. This determines the freq dispersion.

$$T_d = \frac{1}{2\pi} \frac{d\phi}{dt} \quad \text{where } \phi = \text{Transmitted phase.}$$

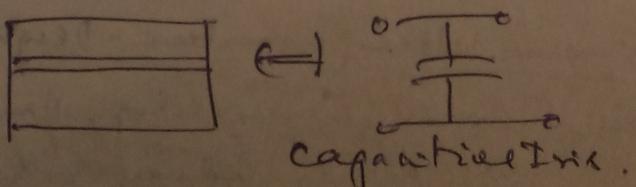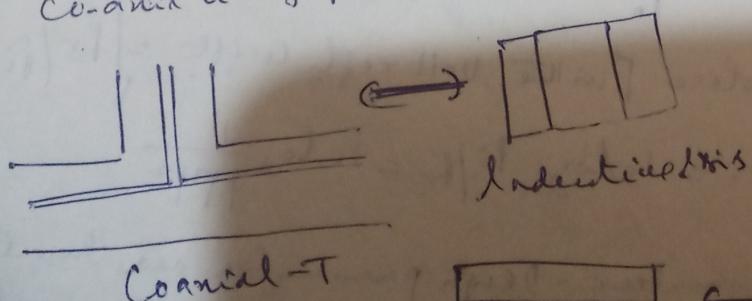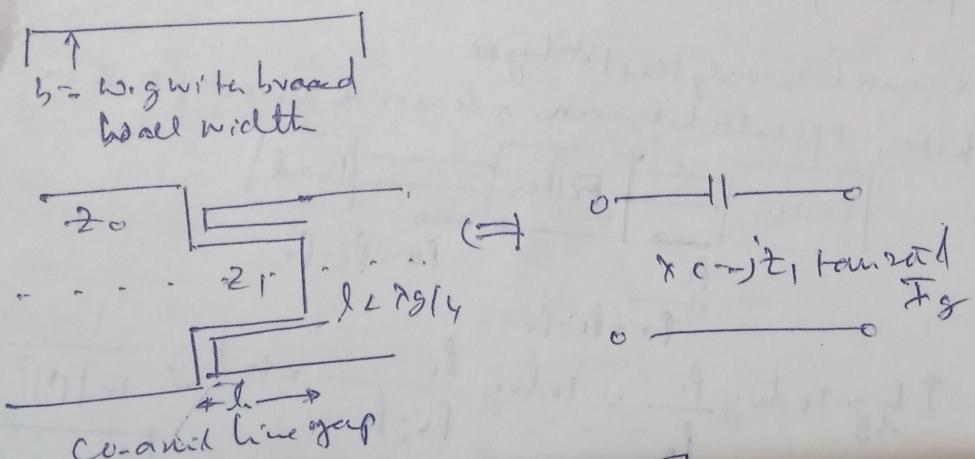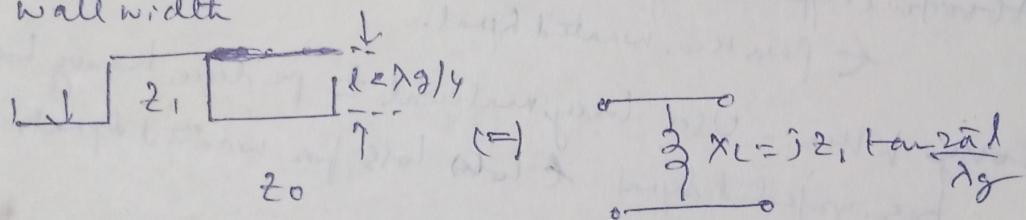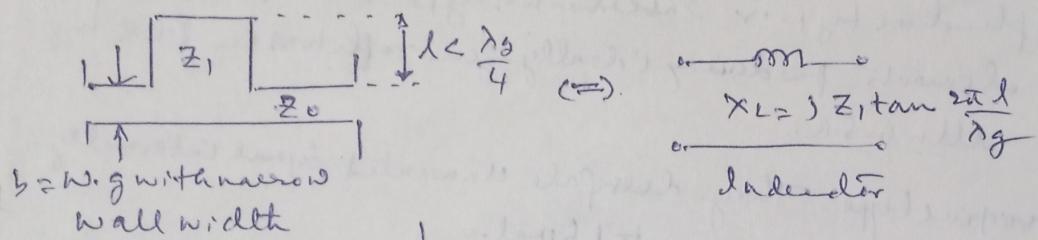Filter elements are realized using a section of wave or coaxial lines or strip or slot lines, or cavity resonators or resonant lines.




I_n
12
 Ω

Steps involved in design of IIR filter by IL method
i.e. select components [MW1-25] 23


1. To design any filter of a particular order of a particular order
Prototype LP filters with design [MW1-21] 23
2. Use frequency transformation to other type of filters.
3. Element Normalization
4. Simulate the elements by using Ladder techniques w.r.t Striplines / wires.

(a) Butterworth filter method:-

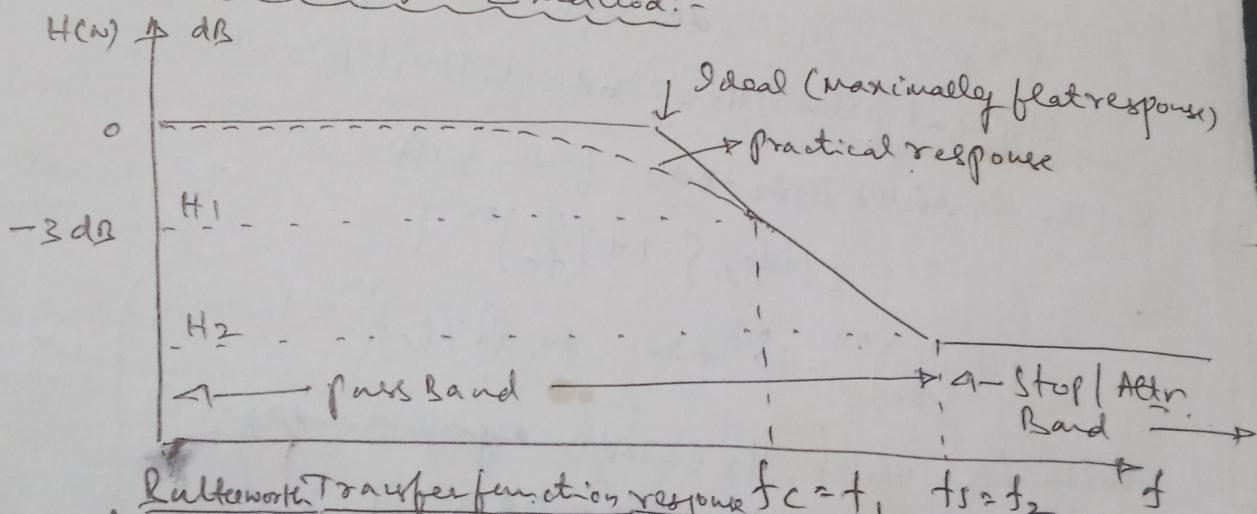

Butterworth Transfer function response $f_c = f_1, f_s = f_2 \rightarrow f$
 $f_c = \text{cutoff freq}, f_s = \text{freq at which stop band gain or atten. in of desired Vallee (i.e. } H_2\text{)}$

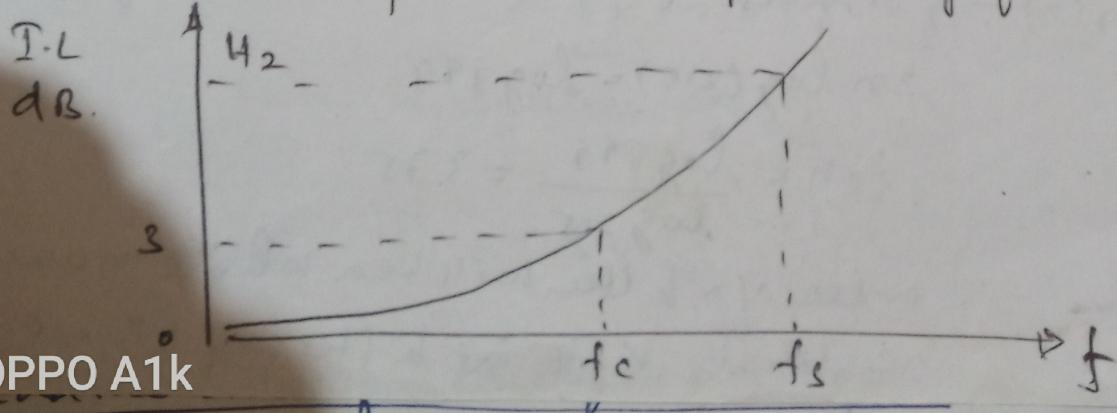Insertion loss response is the complementary of T.F. response ^{or Inversion}



OPPO A1k

CAL

Q.

24

Rutherford's polynomial eqn given by

$$H(f) = 20 \log \left\{ \frac{1}{1 + (f/f_c)^{2n}} \right\}^{\frac{1}{2}}$$

[MWS-22]

f = any freq., f_c = cutoff fr., n = order of the filter

$$H(\omega) = -10 \log \left\{ 1 + (f/f_c)^{2n} \right\} \quad (B)$$

From this order of the filter can be determined.

Eg:- Obtain the order of a low pass filter with

$$\text{pass} = H_1 = -3 \text{ dB} \text{ upto } 4 \text{ kHz } (f_1)$$

stop band atten = $H_2 = -30 \text{ dB}$ to start from 10 kHz

with $f_1 = 4 \text{ kHz}$, $H_1 = -3 \text{ dB}$ from eqn (A)

$$-3 = -10 \log \left\{ 1 + \left(\frac{4}{f_c} \right)^{2n} \right\}$$

$$1 + \left(\frac{4}{f_c} \right)^{2n} = 10^{-0.3} = 2 \quad \text{or} \quad \left(\frac{4}{f_c} \right)^{2n} = 1 \quad (1)$$

With $f_2 = 10 \text{ kHz}$, $H_2 = -30 \text{ dB}$ again from eqn (B)

$$-30 = -10 \log \left\{ 1 + \left(\frac{10}{f_c} \right)^{2n} \right\}$$

$$\therefore \left(\frac{10}{f_c} \right)^{2n} = 1000 \quad (2)$$

$\Rightarrow (2) \div (1)$ gives $\left(\frac{10}{4} \right)^{2n} = 1000$, taking log on both sides

$$2n \log 2.5 = \log 1000$$

$$\therefore n = \frac{\log 1000}{\log 2.5} = 3.75$$

\therefore order of a filter will be a whole number

We select $n = 4$ i.e filter of 4th order


$$\therefore \left(\frac{4}{f_c} \right)^{2n} = 1000 \quad (2)$$

OPPO A1k

chebyshev filter:-

Calculation

I_n

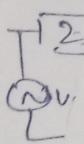

- Design LPF using discrete components
in MW 1-25



23

(b) chebyshev filter method:-
+ The response has some permissible ripples (in dB) in pass band & no ripples in stop band. e.g. $\pm 0.5 \text{ dB}$, $\pm 0.3 \text{ dB}$, $\pm 5 \text{ dB}$ etc.

MW 1-23

21

d.B. $\propto H$.

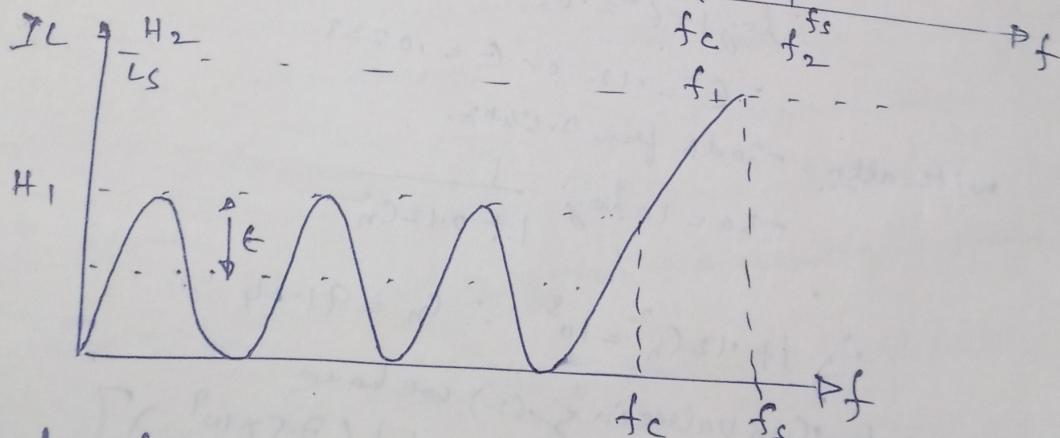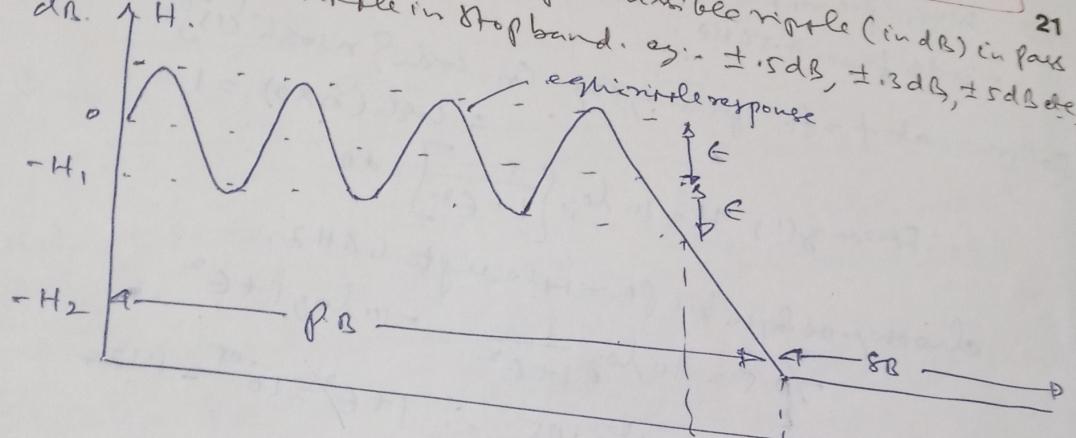

chebyshev polynomial is given by

$$H(\omega) = 10 \log \left\{ \frac{1}{1 + \epsilon^2 C_n^2} \right\} \text{dB} - (1)$$

C_n is chebyshev coefft.

$$\text{where } C_n = \cosh \left\{ n \cosh^{-1}(f/f_c) \right\} - (2)$$

Find the order of a chebyshev filter:-

OPPO A1k

22 Q:- Find the order of a chebychev filter
With ρ -slope $\pm 0.5 \text{ dB}$ upto 4 GHz , atten or IL tube
 -30 dB from 7.5 GHz .

Soln:- at $f = f_c$ from eq(2) $C_n = \cosh^{-1} \left[n \cosh^{-1}(\epsilon) \right]$

$$\therefore \text{From eq(1)} H = 10 \log \left[\frac{1}{1 + \epsilon^2} \right] \text{ dB}$$

choosing ϵ such that ρ -slope upto 4 GHz .

$$-0.5 = 10 \log \frac{1}{1 + \epsilon^2} = -10 \log 1 + \epsilon^2$$

$$\log 1 + \epsilon^2 = -0.05 \quad \therefore 1 + \epsilon^2 = 10^{-0.05} = 1.12$$

$$\therefore \epsilon^2 = 0.12 \quad \text{or} \quad \epsilon = 0.223$$

With atten. -30 dB from 7.5 GHz .

$$-30 = 10 \log \frac{1}{1 + 0.12 C_n^2}$$

$$\therefore 1 + 0.12 C_n^2 = 10^{-3} \quad \therefore C_n = 91.24$$

Substituting this value in eq(2) we have

$$91.24 = \cosh^{-1} \left[n \cosh^{-1} \left(\frac{7.5 \times 10^9}{4 \times 10^9} \right) \right]$$


$$\cosh^{-1}(91.24) \approx n \cosh^{-1}(1.875)$$

$$\therefore n = \frac{\cosh^{-1}(91.24)}{\cosh^{-1}(1.875)} = \frac{5.207}{1.2416} \approx 4.19$$

\therefore we select a filter of order 5.

OPPO A1k

C.I.A. Procedure

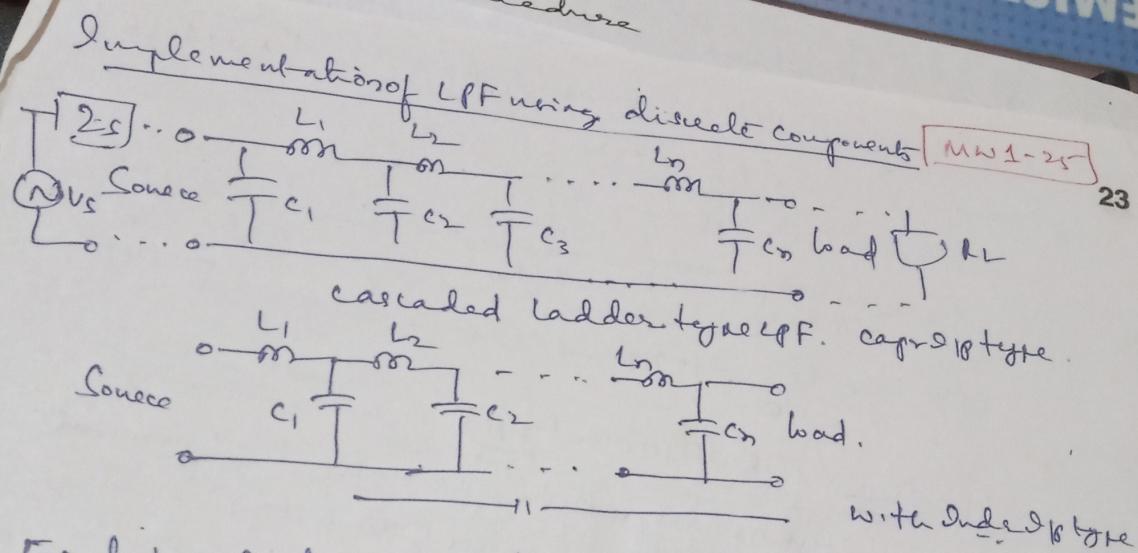


Each L-C Section is a 2nd order LPF, hence two L-C Sections give 4th order. In general $\frac{n}{2}$ Sections (n is even) are needed to construct an n th order filter.

To construct an odd order filter we need cascade required no. of 2nd order filters & a 1st order filter.

e.g.: - 3rd order \rightarrow one 2nd order filter with a first order filter
 5th order \rightarrow two $\text{---} \text{---} \text{---} \text{---}$ etc.

In general $\left(\frac{n-1}{2}\right)$ Sections (where n is odd) are required to cascade with a 1st order filter to construct odd order filter.

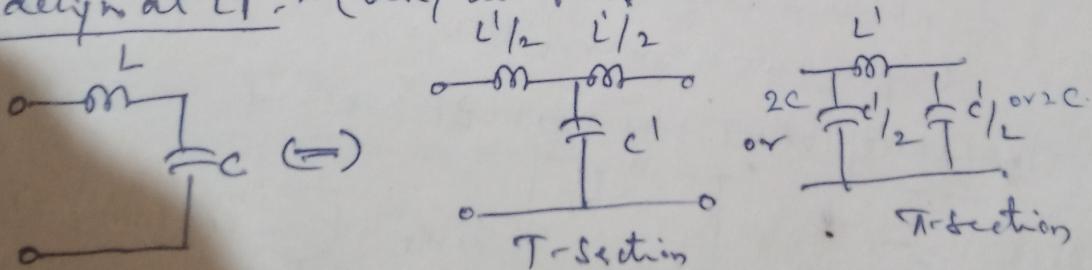Filter design at LF :- (using lumped elements like L, C)



$$\text{If no -char. capac. } = \sqrt{\frac{L}{C}} - (1)$$

$$f_c = \text{cutoff freq. of filter} = \frac{1}{\pi \sqrt{LC}} - (2)$$

24

It is common to split L & C as $L_1/2 + C_1/2$
 Form eq (1) $L^1 = c R_0^2 \quad \text{--- (3)}$

MW 1-26

Eq (3) in eq (2) gives

$$f_C = \frac{1}{\pi R_0 C} \quad \text{or} \quad C = \frac{1}{\pi f_C R_0} \quad \text{or} \quad \frac{C}{2} = \frac{1}{2\pi f_C R_0} = \frac{1}{w_0 R_0} \quad \text{--- (4)}$$

$$\text{Hence } \frac{L^1}{2} = \frac{R_0}{w_0} \quad \text{--- (5)}$$

Practical LPF design (Butterworth type):-

Butterworth filters are designed using normalized polynomials for various values of n (n is the order of the filter).

$$\text{eg:- } n=1 \quad s+1$$

$$n=2 \quad (s^2 + 1.414s + 1)$$

$$n=3 \quad (s^3 + s^2 + 1)(s+1) \text{ etc.}$$

$$\therefore \text{Normalized TF for 2nd order filter is } H(s) = \frac{1}{s^2 + 1.414s + 1}$$


(Normalized means, $f_C = \text{unity}$)

$$\text{or } w_0 = 1$$

$$\text{But actual T.F. is } H(s) = \frac{w_0^2}{s^2 + 1.414w_0 s + w_0^2}$$

coeff. of s term in each of the 2nd order section are used to obtain respective values of components used to implement a given filter.

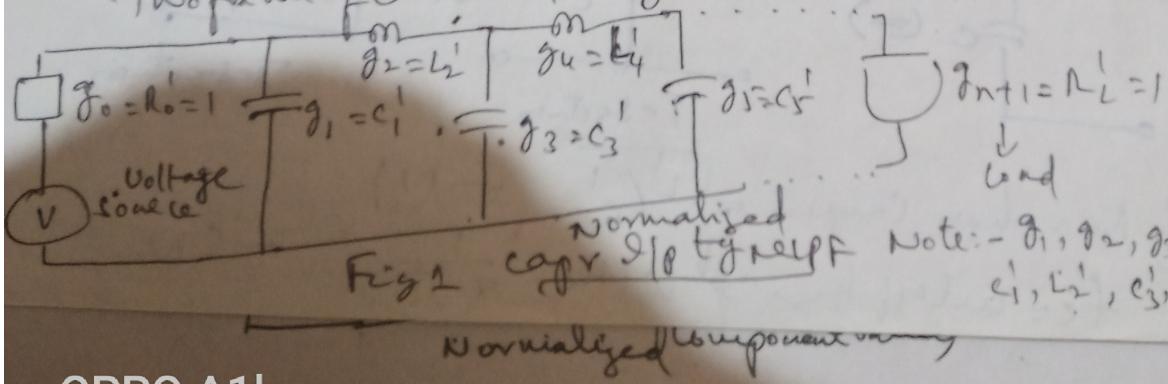Two forms of ladder N/W type LPF are used



OPPO A1k

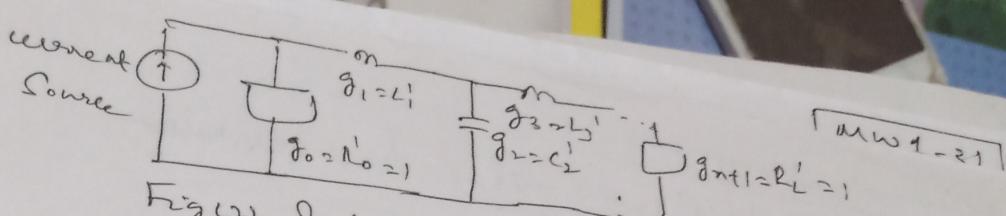


Fig (2) Inductively coupled LP filter
Most of the time we use cap. LP filters.

[MW1 - 21]

[MW1 - 27]

LP filter design: \Rightarrow $Z_0 \rightarrow$ normalized $R_0 = R_{in} = 1$

Elementary filter $(n = \frac{g_n}{w_c R_0}) \quad (1)$ $L_n = \frac{g_n}{w_c} R_0$

From fig 1 g_1, g_3, g_5, \dots are shunt elements (Capacitors)
 g_2, g_4, g_6, \dots series \rightarrow (Inductors)

i.e. in $g(1)$ n is odd such that $n = 1, 3, 5, \dots$
 \rightarrow even $\rightarrow n = 2, 4, 6, \dots$

Q: Obtain the component of the 4th order Butterworth filter with $f_c = 4kHz, R_0 = 50\Omega$


$$T.F. \text{ is } H(s) = (s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$$


\therefore coefficients in the above equation are $g_1 = g_3 = 0.765, g_2 = g_4 = 1.848$

These are the normalized component values

$$\text{i.e. } g_1(C_1') \leftarrow g_3(C_3') ; g_2(L_2') \leftarrow g_4(L_4')$$

\therefore The values from $g_2(L_2') = 1.848 \quad g_4(L_4') = 1.848$

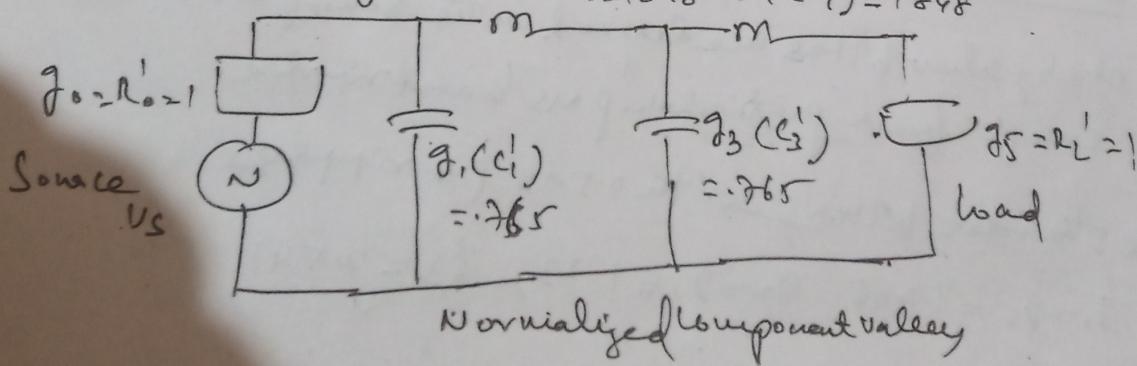

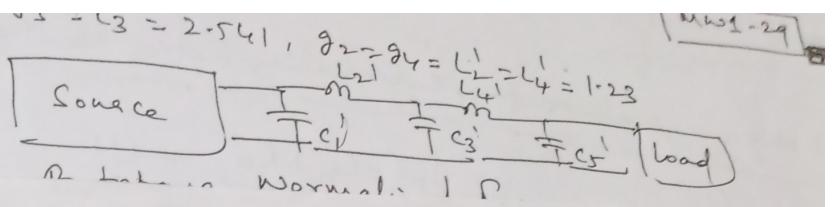


MW 1
28

De-normalized Components:-

$$c_1 = c_3 = \frac{(C_1 \text{ or } C_3) \text{ or } (g_1 \text{ or } g_3)}{\text{co-cho}} \quad f_{c} = 4 \text{ kHz, Resonance}$$

$$\therefore c_1 = c_3 = 0.609 \mu\text{F}$$
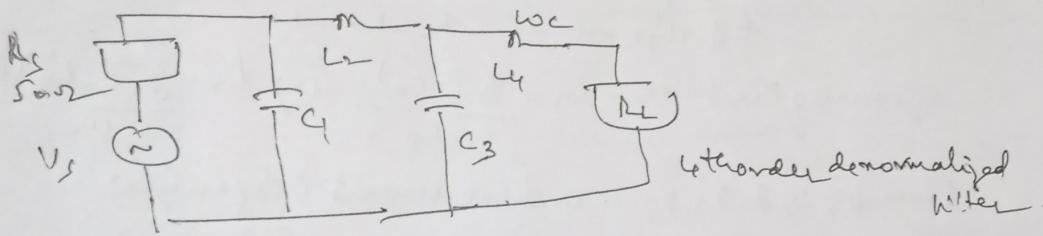
$$11) \quad L_2 = L_4 = \frac{(L_2 + L_4) \text{ or } (g_2 \text{ or } g_4) R_o}{R_o} = 3.62 \text{ mH}$$



fixed values

$$\frac{3}{R_o} = 2.02 \mu\text{F}$$

Note:- Instead of T.F we can use Normalized Component table available in log books.

order

$$n=1 \quad g_0=1 \quad g_1=2 \quad g_2=1.0$$

$$g_1=g_2=1.414 \quad g_3=1.0$$

$$n=2 \quad \rightarrow \quad g_1=g_2=1.414 \quad g_3=1.0$$

$$g_1=1, g_2=2, g_3=g_4=1$$

$$n=3 \quad \rightarrow \quad g_1=g_3=0.707, g_2=g_4=1.8478, g_5=1$$

$$g_1=g_3=0.707, g_2=g_4=1.8478, g_5=1$$

$$n=4 \quad \rightarrow \quad g_1=g_3=0.707, g_2=g_4=1.8478, g_5=1$$

Note:- chebychev filters are designed in the same fashion except for a particular pass band ripple.

H.W

Q:- For 5th order filter with 0.5dB p.b. ripple

$$g_1=g_5=1.706, g_2=g_4=1.23, g_3=2.541$$


$$\frac{1}{2} \frac{1}{2\sqrt{1+12x}}$$

with $f_{cst.} = 1.044$

Soln. $g_1 = g_5 = c_1^+ = c_5^- = 1.706$

MW1-29
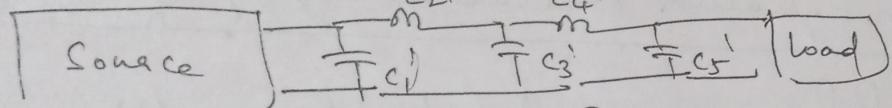
$$g_3 = c_3^+ = 2.541, g_2 = g_4 = \frac{L_2}{L_4} = 1.23$$




Prototype Normalized Form

At $f_c = 4\text{GHz}$, $R_o = 50\Omega$, Denormalized Values are


$$c_1 = c_5 = \frac{g_1 \omega R_o}{\omega c R_o} = 1.86 \text{ pF}, c_3 = \frac{g_3}{\omega c R_o} = 2.02 \text{ pF}$$
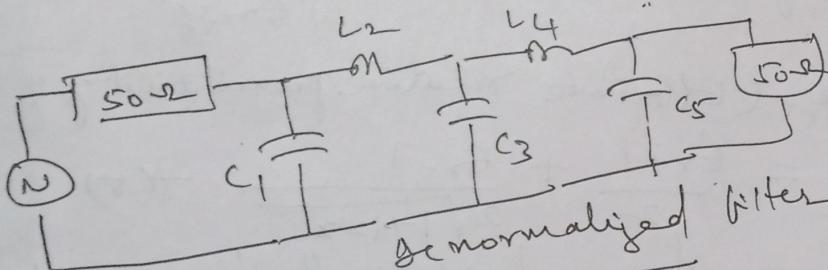
$$L_2 = L_4 = \frac{g_2 g_4 R_o}{\omega c} = 2.447 \text{ nH}$$




Prototype Denormalized Filter

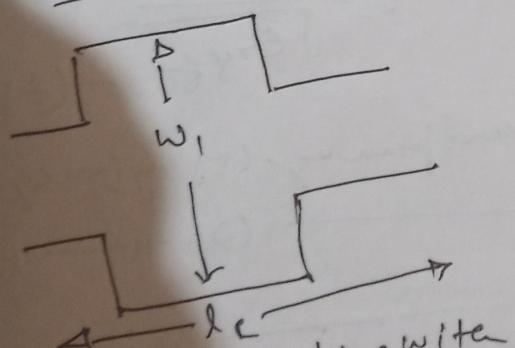Practical realization of Geneva strip line filters



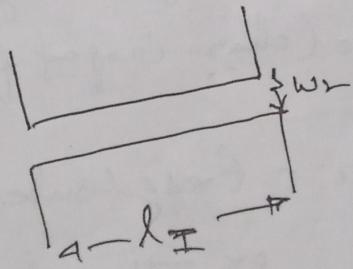wider strip line with
low impedance acts
as a capacitor



narrow strip line having
high impedance
acts as an inductor

OPPO A1k

$$\text{Width} = \frac{\lambda}{2} = 2\sqrt{1+12}(1.044)$$

Dimension in between C & L acts as a resistor.

[Ans 1-30]

Design equations for calculating length of strip line

$$\beta l_n(\text{incident}) = \frac{g_n (= L_n)}{R_0} - (1)$$

$$\beta l_n(\text{cap}) = \frac{g_n (= C_n) Z_{\text{low}}}{R_0} - (2)$$

where $\beta = \text{phase constant} = 2\pi/\lambda_g$: radians

$$\lambda_g = \text{wavelength} = \frac{\lambda}{\sqrt{\epsilon_{\text{eff}}}} - (4)$$

ϵ_{eff} (Effective relative permittivity of stripline)

$$= \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2\sqrt{1+12x}} - (5)$$

$$\text{where } x = \frac{h}{w} = \frac{\text{height of stripline}}{\text{width}} - (6)$$

typically $x \approx 1.044$

$$R_0 (\text{characteristic impedance of strip line}) \approx \frac{Z_0}{\sqrt{\epsilon_{\text{eff}}}} \ln\left(8x + \frac{1}{4x}\right) - (7)$$

Note: - ϵ_{eff} can be found from eq (5) by binay trial or \rightarrow

e.g.: - Implement stripline of Butterworth filter (4th order)

Data: - $R_0 = 50\Omega$, $Z_{\text{high}} = 150\Omega$, $Z_{\text{low}} = 10\Omega$,

Passband atten. \rightarrow $\epsilon_r = 5$, $h = 0.5\text{mm}$ \rightarrow I.L
 $H_1 = -3\text{dB}$ upto 4GHz, $H_2 = -30\text{dB}$ from 10GHz

WTF: Procedure

Selection

$$* \epsilon_{\text{eff}} = \frac{\epsilon_2 + 1}{2} + \frac{\epsilon_{2x} - 1}{2\sqrt{1 + \epsilon_{2x}}}$$

with $\epsilon_{2x} = 25, x = 1.044$

MW1- 35
MW1-31

$$\epsilon_{\text{eff}} = \frac{5+1}{2} + \frac{5-1}{2\sqrt{1+\epsilon_{2x}(1.044)}} = 3.54$$

$$* \lambda = \frac{c}{f} = \frac{3 \times 10^8}{4 \times 10^9} = 0.075 \text{ m}$$

$$* \lambda_g = \frac{\lambda}{\sqrt{\epsilon_{\text{eff}}}} = \frac{0.075}{\sqrt{3.54}} = 0.02 \text{ m}$$

$$\therefore * \beta = 2\pi/\lambda_g = 61.625 \text{ rads}$$

For 4th order LP B-w filter, coeffts. are

$$g_1 (= c_1') = g_3 (= c_3') = 2.65 \text{ units}$$


$$g_2 (= l_2') = g_4 (= l_4') = 1.848 \text{ units}$$

w.k.t $B_{l_n(\text{cap})} = \frac{g_n (= c_n')}{R_o} \text{ low when n is odd}$

$$\therefore l_1 \text{ or } l_3 = \frac{2.65 \times 10}{50} = .0025 \text{ m} \quad \text{length cap: strip lines}$$

$$(1) \quad B_{l_n(\text{load})} = \frac{g_n (= l_n') R_o}{Z_{\text{high}}} = \frac{1.848 \times 50}{150}$$

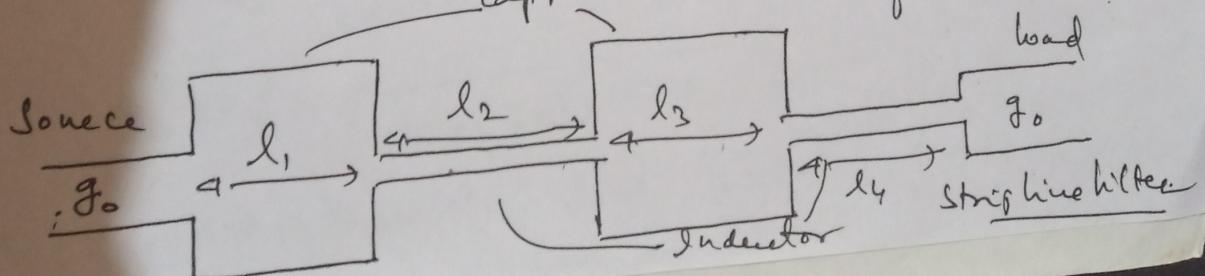
$$\therefore l_2 \text{ or } l_4 = .01 \text{ m} \quad \text{length Inductor strip lines}$$



$$\omega = \frac{h}{n} = .479 \text{ mm}$$

Generally $t = 1 \text{ mil} = .0254 \text{ mm}$

MW 1-32

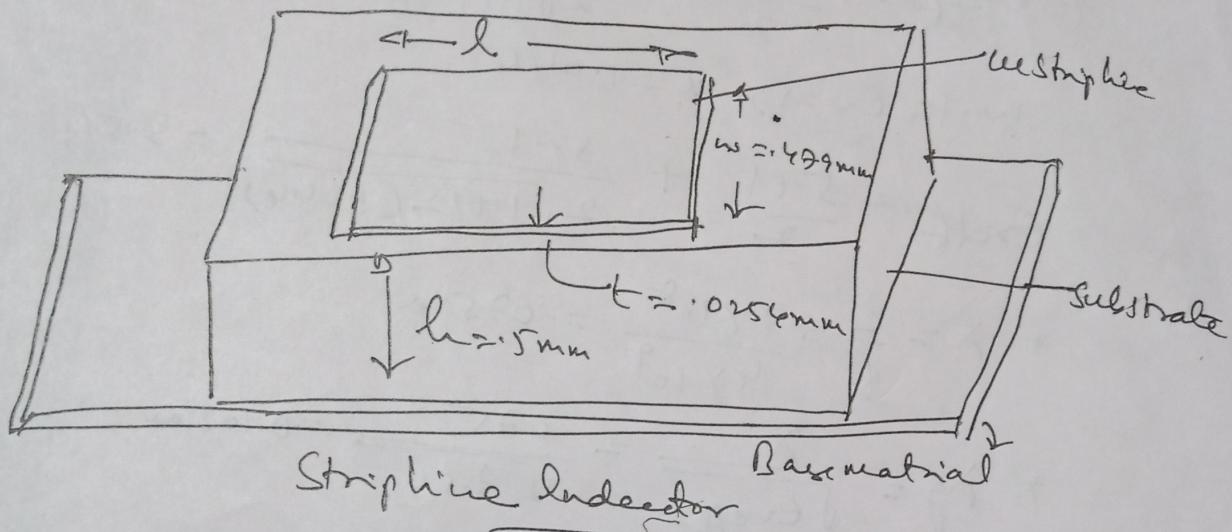

Summary of BP or chebyshev LP filter design

- 1). Find order of tee filter
- 2). Realize a prototype normalized filter
- 3). $\frac{-11}{-1}$ de $\frac{-11}{-1}$
- 4). Find β & α_{eff} , determine 'l' of cap & inductor striplines.

109

LPT to BPF: Procedure

LP Microwave filter design:-

MW1- 35

- * Find order of filter from f_1, f_2, I . Linfield I. Lin & my R. nor chebyshev T.F.
- * Realize prototype Normalized / de-normalized filter using filter coeff's from T.F or Table
- * Realize Stripline filter by converting prototype filter

MW1-33



H.P filter design:- * Direct design not possible

* first realize LP as above

* Convert LP to HP using equations

* Realize new strip lines as in LPF.

e.g.: - 4th order LPF

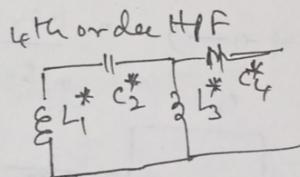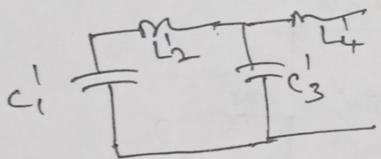

cap → inductance & vice-versa

Design equations:- $L_n^* = \frac{R_o}{\omega_c c_n^*} \quad (1)$ $n \text{ is odd } 1, 3, 5, \dots$

$$c_n^* = \frac{1}{\omega_c R_o L_n^*} \quad (2) \quad n \text{ is even } 2, 4, 6, \dots$$

$R_o = 50 \Omega, f_c = 4 \times 10^9 \text{ Hz}$

e.g.: - 4th order B.W H.PF:-

$$g_1 (= c_1^*) = g_3 (= c_3^*) = 0.765$$

$$g_2 (= l_2^*) = g_4 (= l_4^*) = 1.848$$

Prototype + denormalized:

$$L_1^* = L_3^* = \frac{50}{2\pi \times 4 \times 10^9 \times 0.765} =$$

$$c_2^* = c_4^* = \frac{1}{2\pi \times 4 \times 10^9 \times 1.848} =$$

Stripline:- $R_o = 50 \Omega, Z_{high} = 150 \Omega, Z_{low} = 10 \Omega, \epsilon_r = 5, f_c = 4 \text{ GHz}$

- i.e. Procedure

MW1 - 35

$(c_2 - l_2)$
n.o.d.F

MW1-34


$$\beta_{ln(\text{indeed})} = \frac{q_n (= c_n^l) R_o}{z_{\text{high}}} \quad n \text{ is odd } 1, 3, 5, \dots$$

$$\beta_{ln(\text{cap})} = \frac{q_n (= k_n^l) z_{\text{low}}}{R_o} \quad n \text{ is even } 2, 4, 6, \dots$$

$$t_{\text{eff}} = 3.54, \quad \lambda = 0.75 \mu\text{m}, \quad \lambda_g = 0.04 \mu\text{m}, \quad \beta = 157.1 \text{ rad/s}$$

$$\therefore l_1 = l_3 (\text{Indeed-Straightline length}) = \frac{0.765 \times 50}{157.1 \times 150} = \text{mm}$$

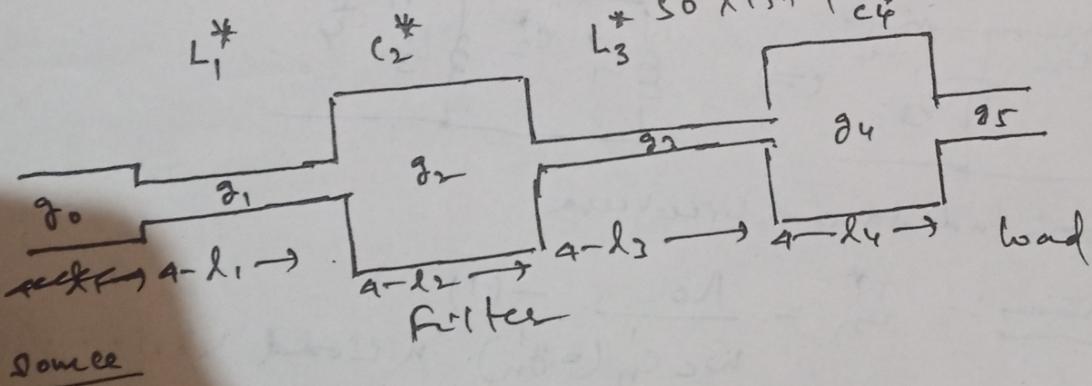
$$l_2 = l_4 (\text{Cap-11-}) = \frac{1.848 \times 10}{50 \times 157.1 \text{ cm}}$$



LPF to BPF: Procedure

- Realize LPF (Prototype)
- Convert Series L_2' of LPF to Series L-C Ckt by BPF

MW1 - 35

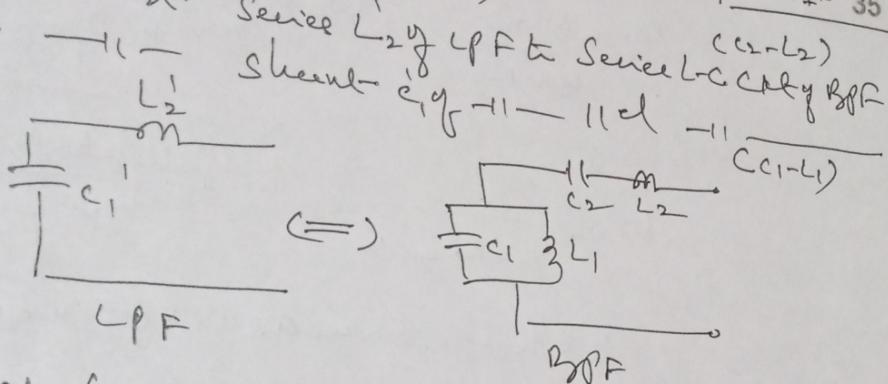

- If f_{c1} is cutoff freq LPF, f_{c2} is cutoff freq HPF
For BPF $f_{c2} > f_{c1}$

Design equations:-

- Components of shunt reactance

$$C_n = \frac{C_n}{w_r R_0 \Delta}, \quad L_n = \frac{\Delta R_0}{w_r C_n} \quad \boxed{\text{misold}}$$

- Components of series reactance


$$C_n = \frac{\Delta}{w_r R_0 L_n}, \quad L_n = \frac{L_n R_0}{w_r \Delta} \quad \boxed{\text{misunder}}$$

where $\Delta = \text{fractional bw} = \frac{f_{c2}-f_{c1}}{f_r} \quad \text{for transfer}$

LPF to BEF Procedure

- Realize LPF (Prototype)
- Convert Series L_2' of LPF to shunt L-C Ckt (L_2-C_2)

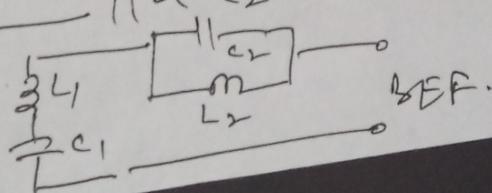- Convert Series C_2' of LPF to shunt L-C Ckt (L_1-C_1)



Design equations

$$C_n = \frac{D C_n'}{w_r R_0}, L_n = \frac{R_o}{w_r C_n' D} \quad \text{for ferroic case}$$

n is odd

$$C_n = \frac{1}{w_r R_o L_n' D}, L_n = \frac{L_n' R_o D}{w_r} \quad \text{for 111 cl case}$$

n is even

Δf_f are same as in BPF except $f_{c1} > f_{c2}$

where f_{c1} is cutoff freq BPF

$$\ell f_{c2} \rightarrow \text{LPP} \quad \ell g = \frac{f_{c1} - f_{c2}}{f_r}$$