

## Experiment 1 - Flat Top Sampling

### Aim:

To design and demonstrate the working of the flat top sampling circuit for a Hz. message signal. Demonstrate the effect of (a) under sampling (b) over sampling (c) right sampling.

### Components Required:

Transistor (SL 100, SK 100), Resistors, Capacitors, Op-amp.

### Theory:

In the sampling process, an analog signal is converted into a corresponding sequence of samples that are usually spaced uniformly in time.  $g(t)$  is necessary so that we can choose the sampling rate properly, so that the sequence of samples uniquely defines the original analog signal.


### *Sampling Theorem:*

A band limited signal of finite energy, which has no frequency components higher than 'W' hertz, may be completely recovered from the knowledge of its samples taken at the rate of  $2W$  samples per second.


### *Quantizing:*

Representing the analog sampled values by a finite set of levels is called quantizing i.e., it converts continuous amplitude samples to a discrete amplitude samples. Sampling Converting a continuous time signal to a discrete time signal.


## Circuits:

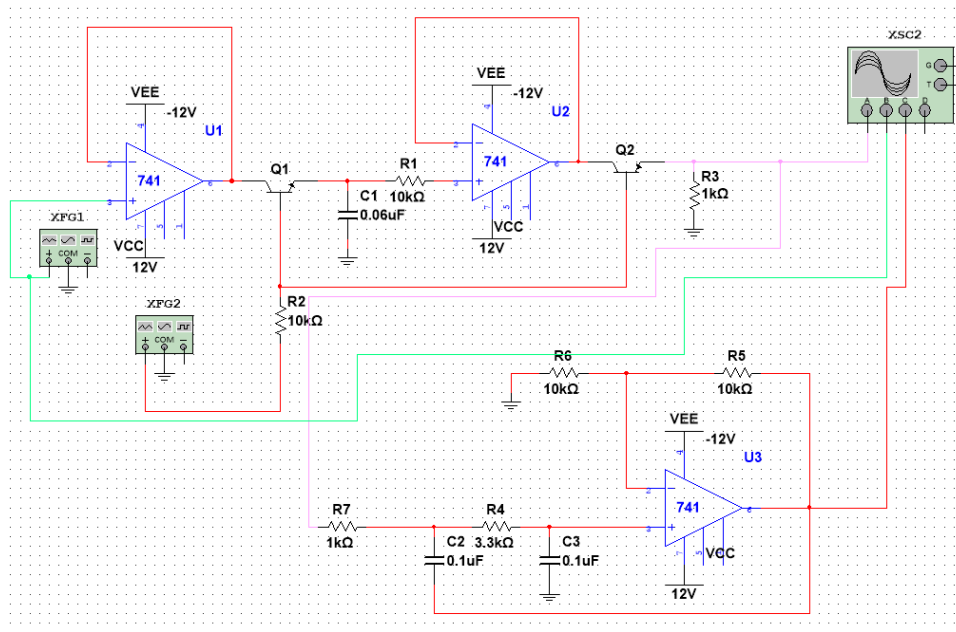

Schematic in Multisim

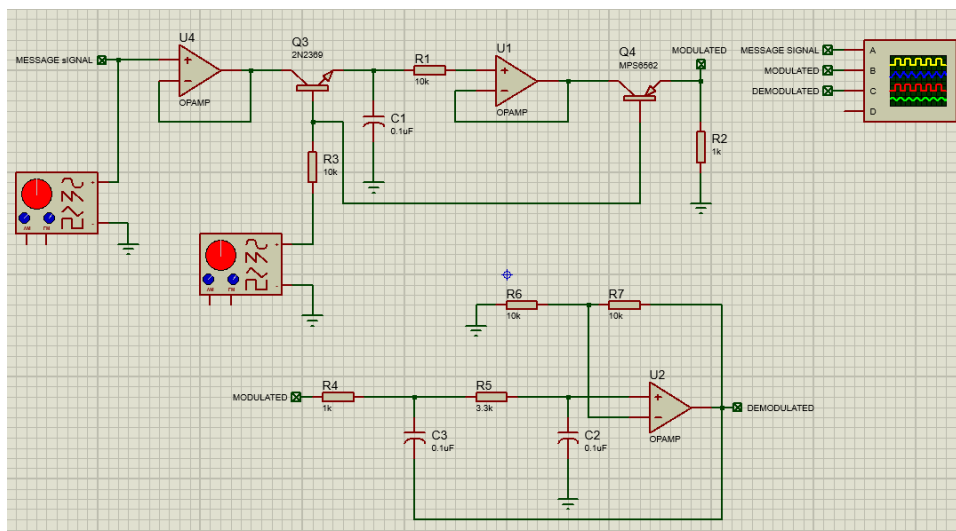


Schematic in Proteus

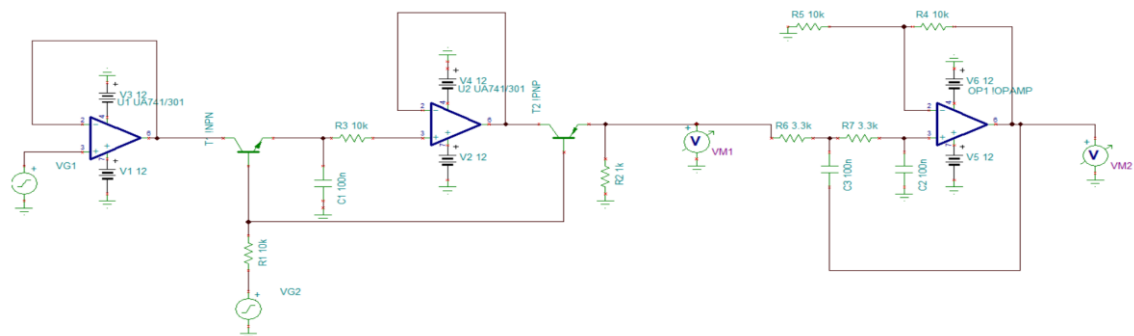


Schematic in Tina


Waveforms:

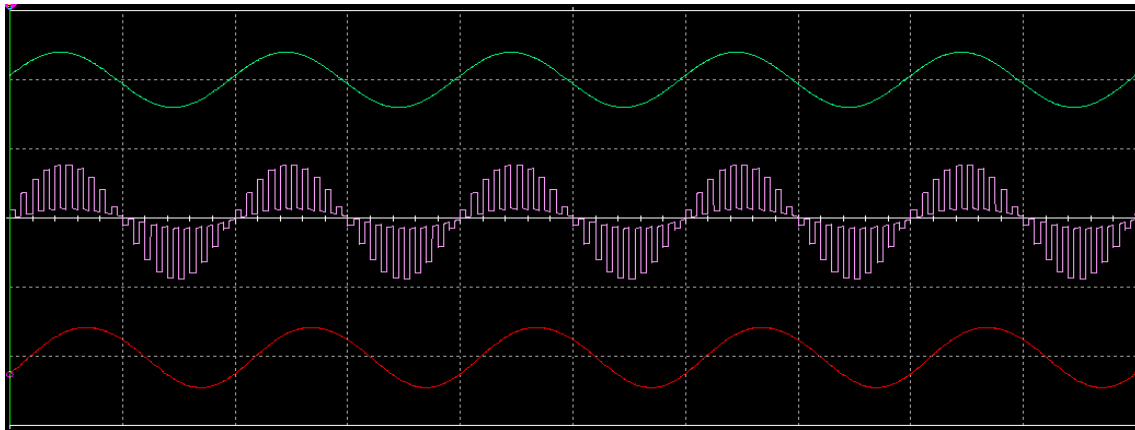

Output Waveforms in Multisim

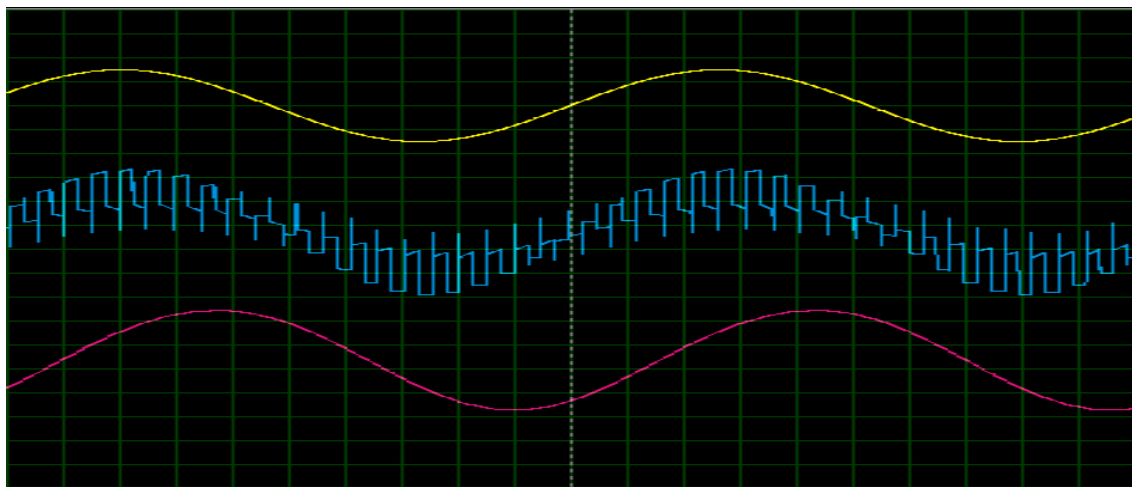

Output Waveforms in Proteus

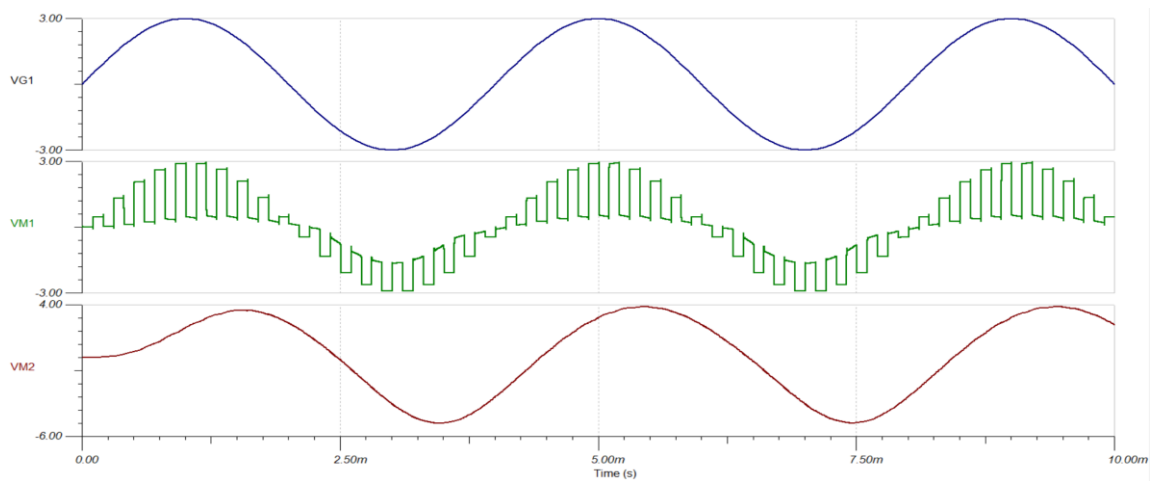

Output Waveforms in Tina

### Applications:

Sampling theorem serves as the basic for the interchangeability of analog signals and digital sequences, which is so valuable in digital signal processing, and digital communications.

## Experiment 2 - Time Division Multiplexing

Aim:

To design and demonstrate the working of TDM and recovery of two band limited signals of PAM signals.

Components Required:

Transistors—SL100, SK100, Resistors, Op-amp


Theory:

TDM is a technique used for transmitting several message signals over a communication channel by dividing the time frame into slots, one slot for each message signal. This is a digital technique in which the circuit is highly modular in nature and provides reliable and efficient operation.


There is no cross talk in TDM due to circuit non-linearities since the pulses are completely isolated. But it also has its disadvantages, which include timing jitter and synchronization is required.

In pulse-amplitude modulation, the amplitude of a periodic train of pulses is varied in proportion to a message signal. TDM provides an effective method for sharing a communication channel.


Circuits:

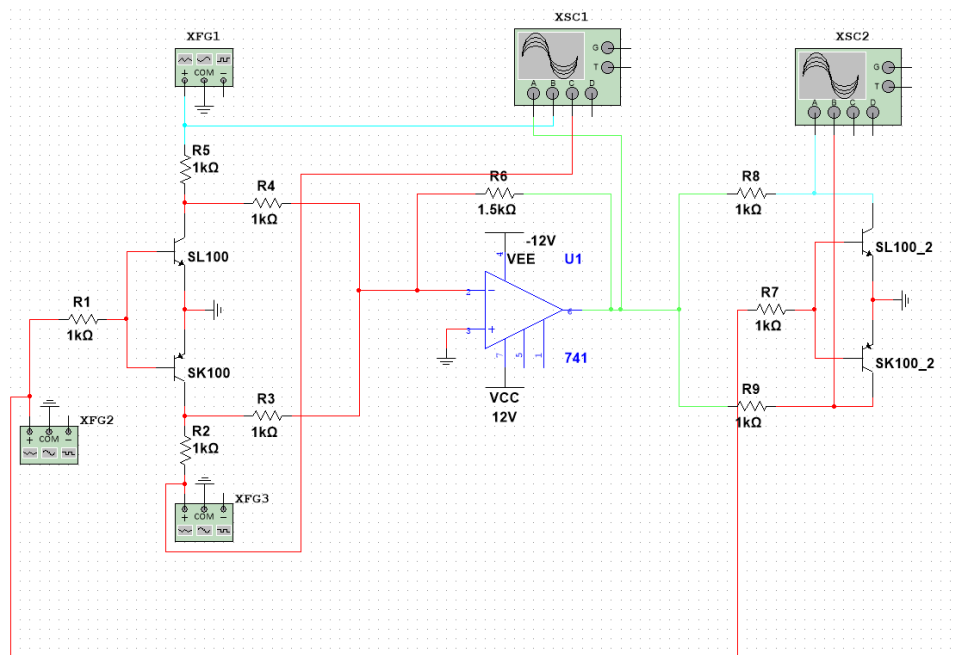

Schematic in Multisim


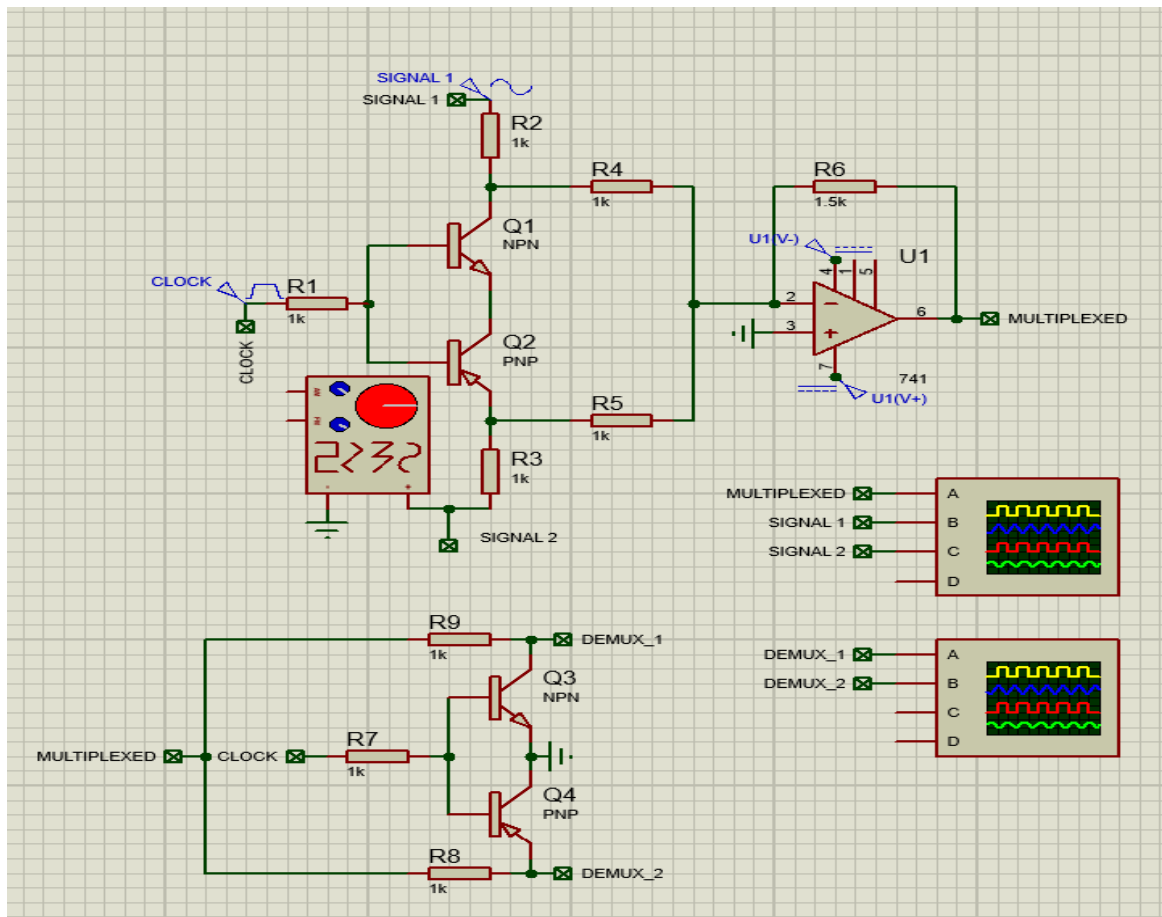


## Schematic in Proteus

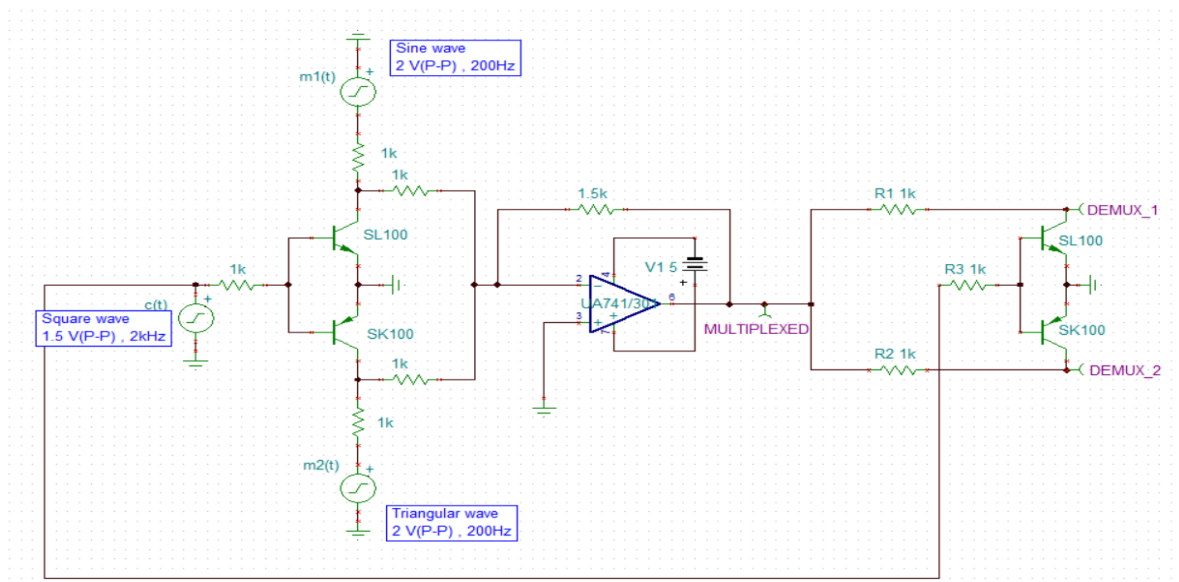



## Schematic in Tina

Waveforms:

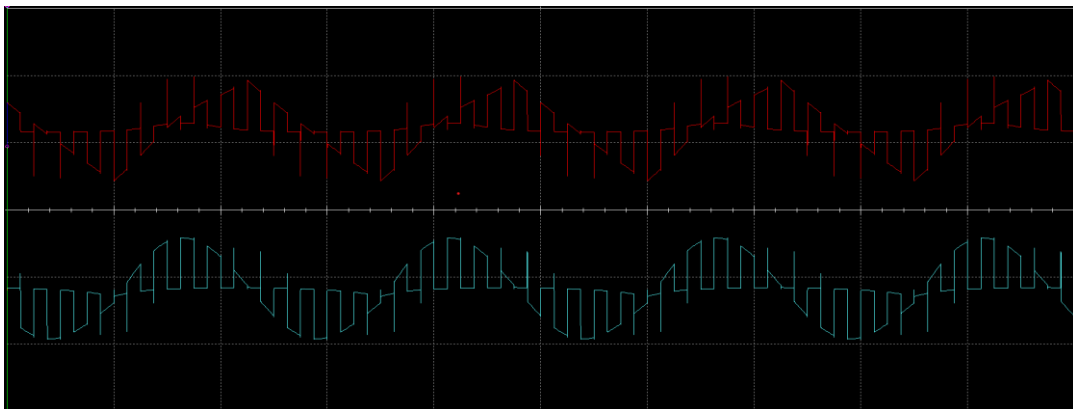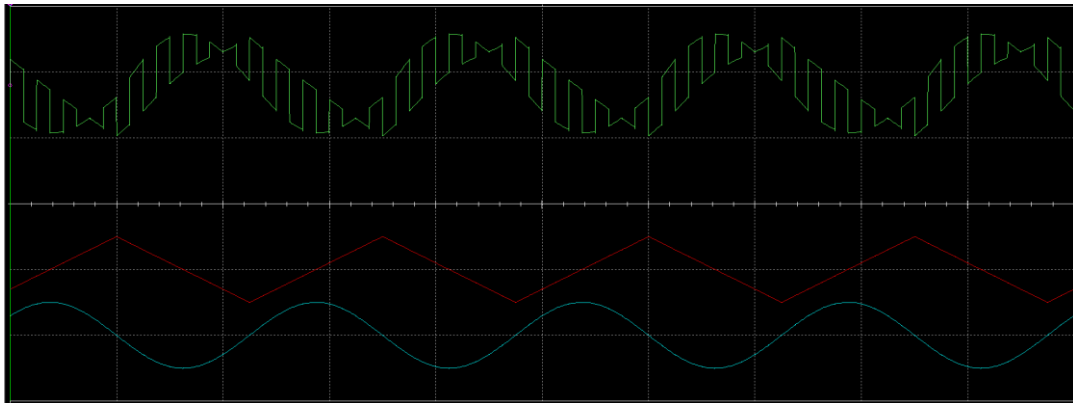


Output Waveforms in Multisim

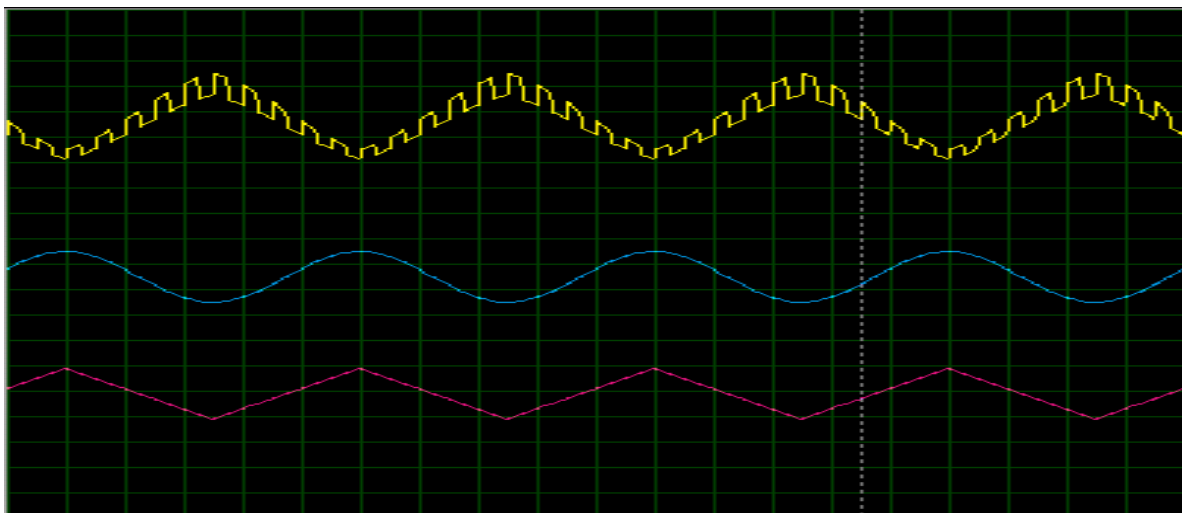

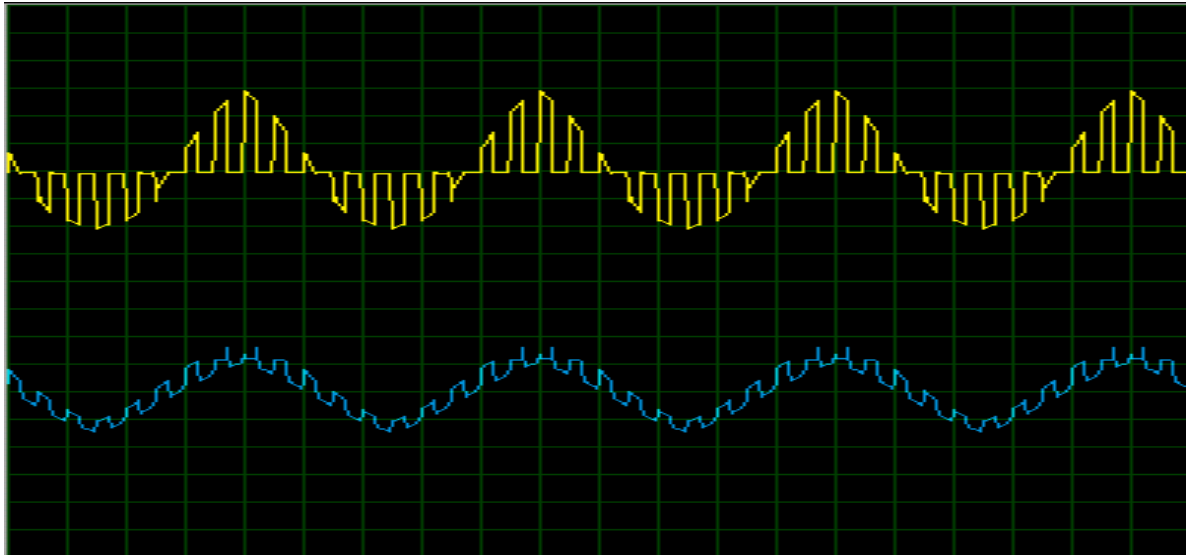

Output Waveforms in Proteus

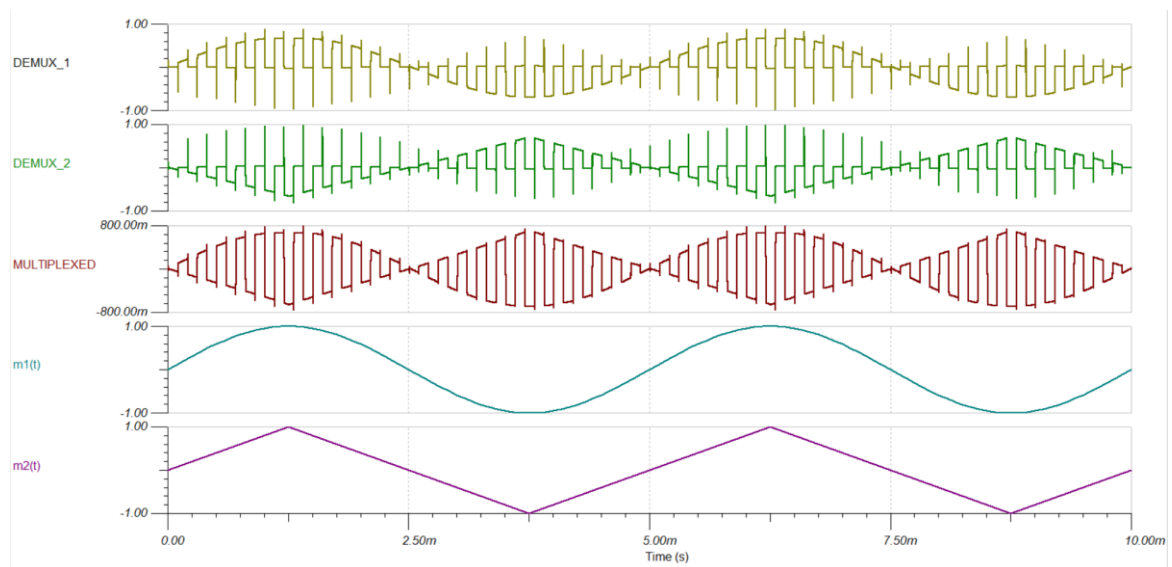

Output Waveforms in Tina

### Applications:

- Single Line Communication
- Telephonic Communication



## Experiment 3 - Amplitude Shift Keying (ASK)

Aim:

To design and verify the operation of ASK generator and demodulator.


Components Required:

Transistor SL100, Resistors, Potentiometers, Op-amp, Diode-BY127


Applications:

Digital data communication for a large number of low-frequency RF applications.


Circuits:

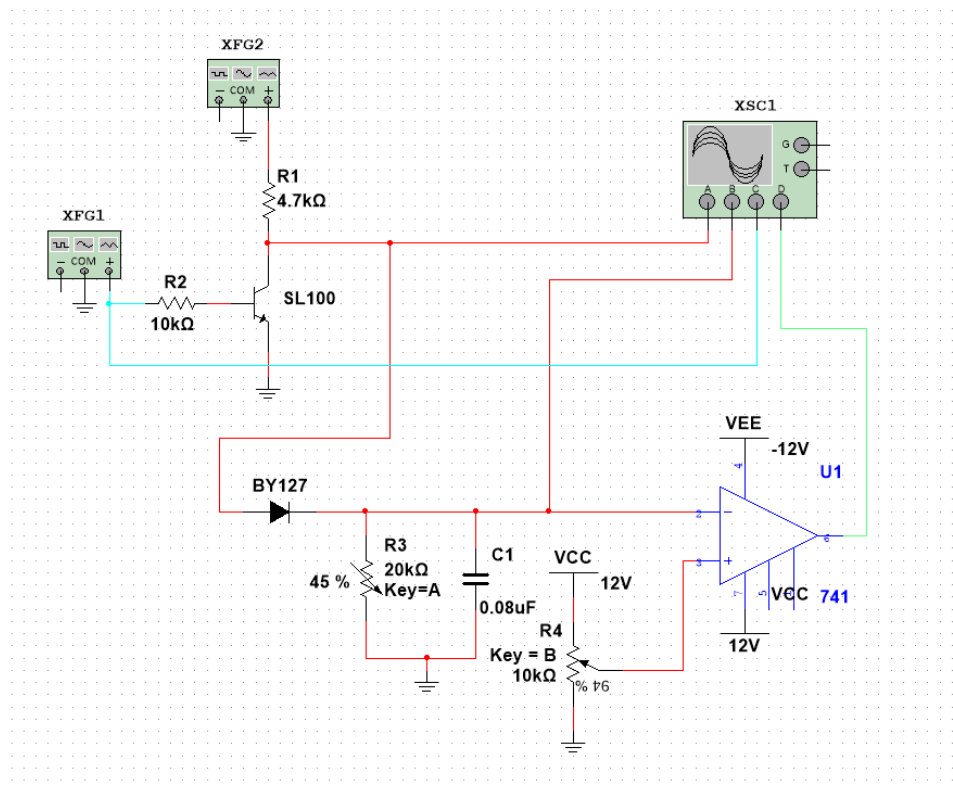

Schematic in Multisim

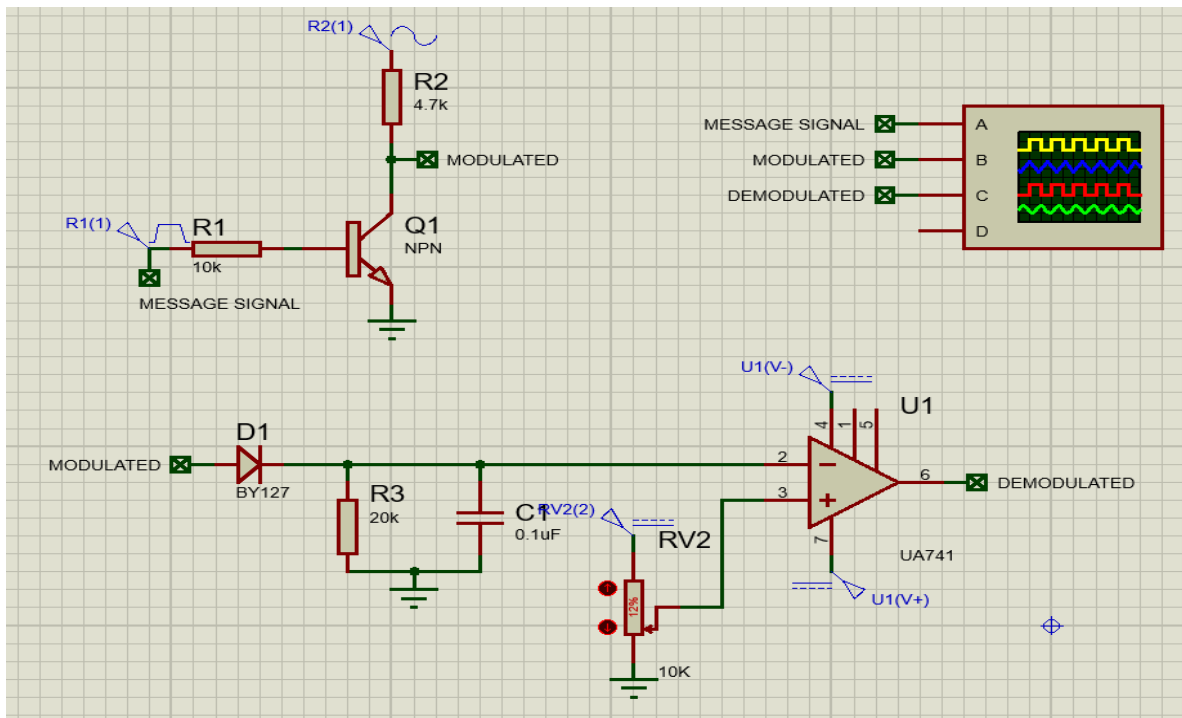


Schematic in Proteus

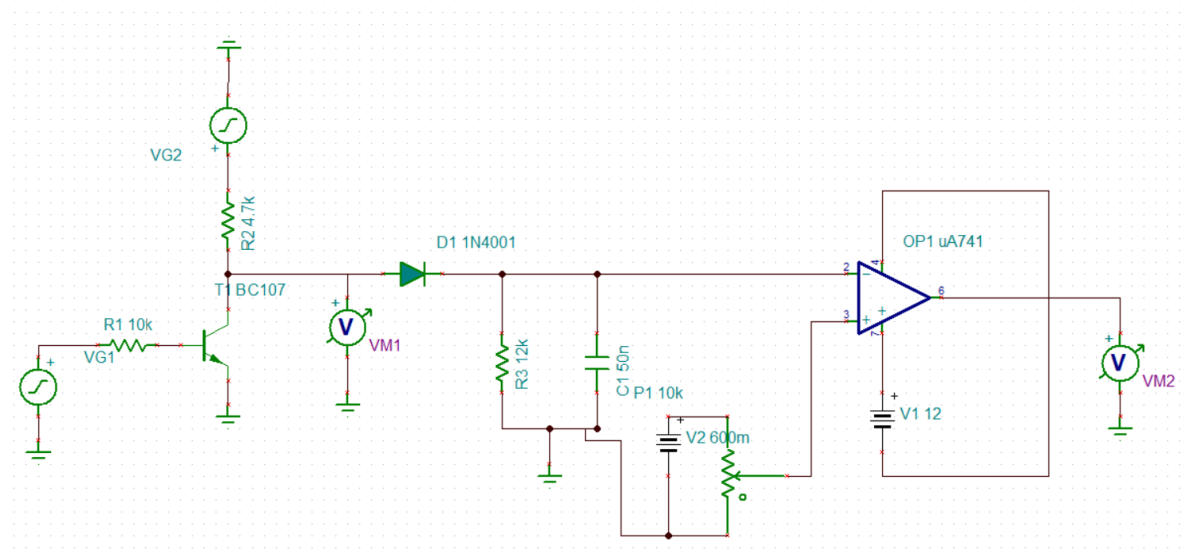


Schematic in Tina


Waveforms:

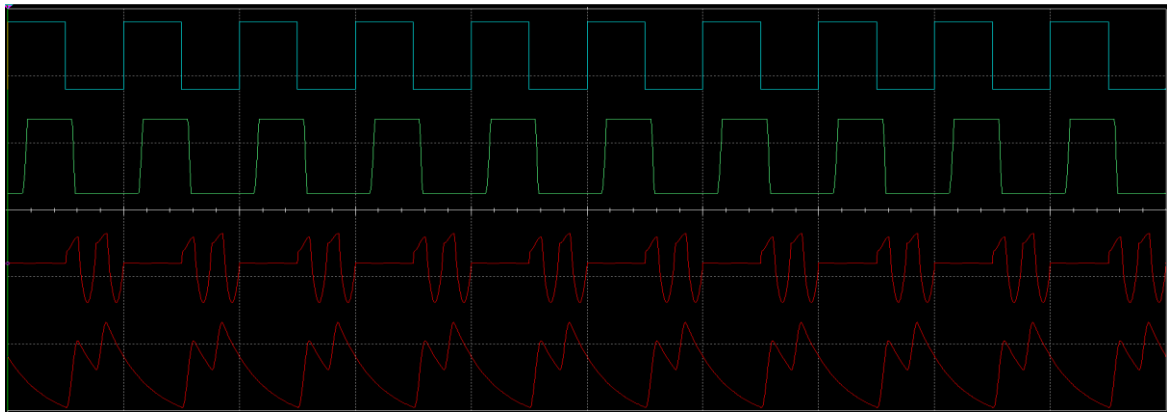

Output Waveforms in Multisim

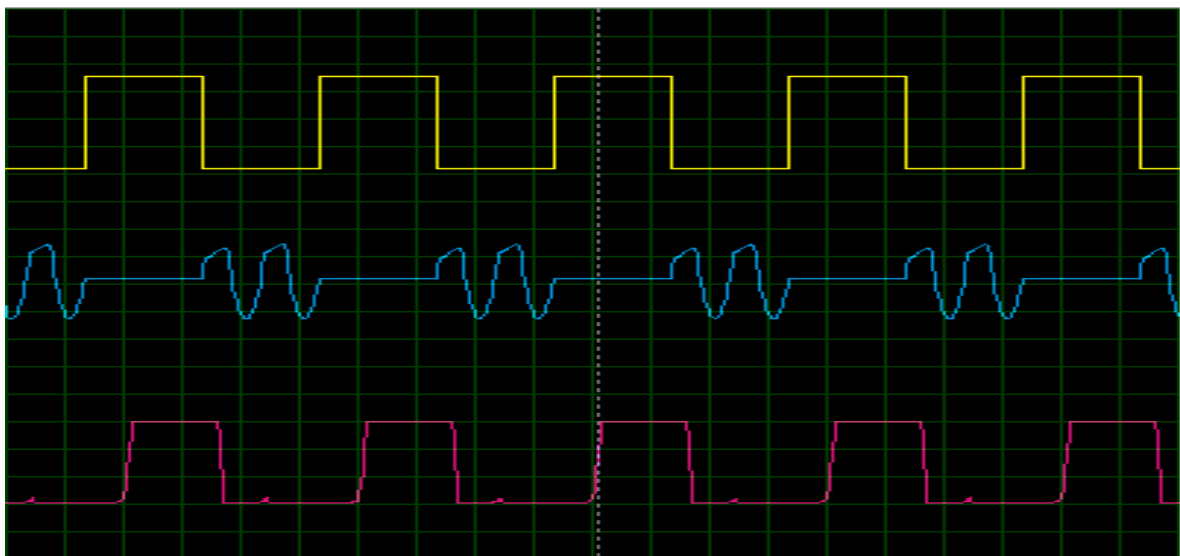

Output Waveforms in Proteus

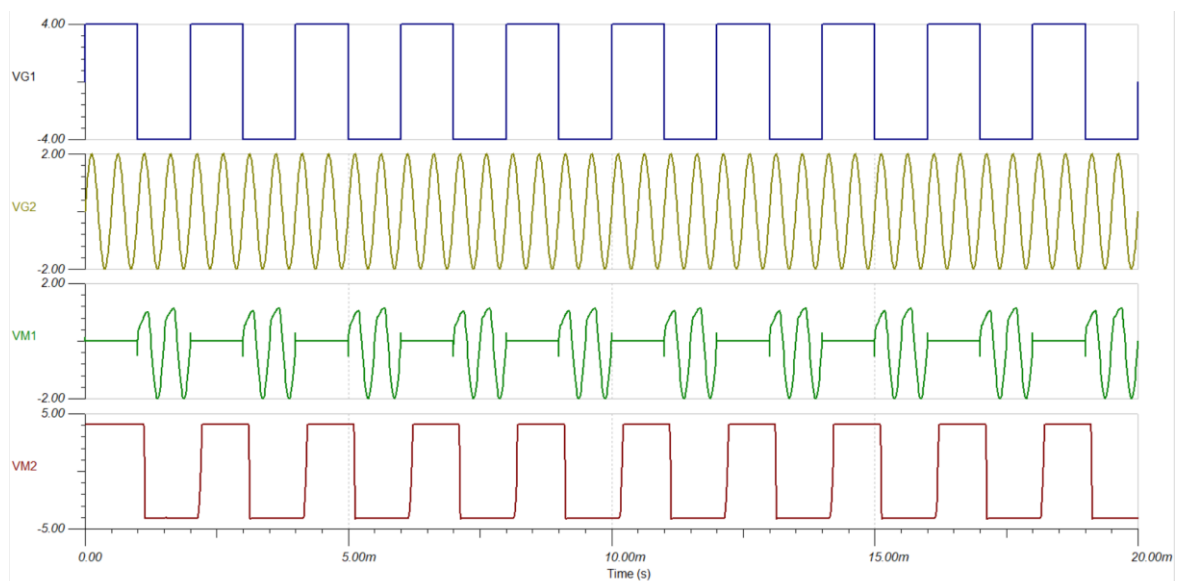

Output Waveforms in Tina